

Digital Integrated Circuits

Chapter 6 – The CMOS Inverter

Contents

- Introduction (MOSFET models) 0, 1st, 2nd order
- The CMOS inverter : The static behavior:
 - DC transfer characteristics,
 - Short-circuit current
- The CMOS inverter : The dynamic behavior
- Energy, power, and energy delay

Introduction - 1

Zero-order model (**ideal switch**)
of n- and p-channel MOSFETs

 


FIG 1.9 Transistor symbols and switch-level models


Inverter

What for a signal between “0” and “1”?



Introduction - 2

First-order model of a MOSFET

Non ideal switch

 


An MOS Transistor

  

What's the value of R_{on} ? Abrupt transition from on to off?

Introduction - 3


The MOS Transistor

 


Source: Rabaey

Introduction - 4

MOS Transistors – n- and p-channel

 



NMOS Enhancement

 

PMOS Enhancement

Introduction - 5



I-V Relations Long-channel n-MOST

  

Source: Rabaey

Introduction - 6

I-V Relations Long-channel p-MOST

  

Source: Rabaey

Introduction - 7

Linear Region: $V_{DS} \leq V_{GS} - V_T$

$$I_D = k'_n \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right) (1 + \lambda V_{DS})$$

with

$$k'_n = \mu_n C_{ox} = \frac{\mu_n \epsilon_{ox}}{t_{ox}}$$

Process Transconductance
Parameter

Saturation Mode: $V_{DS} \geq V_{GS} - V_T$

$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Channel Length Modulation
↙


Introduction - 8

I_D versus V_{GS}

Saturation mode: $V_{DS} > V_{GS} - V_T$


$$V_{DS} = 2.5 \text{ V} \quad V_T = 0.5 \text{ V} \quad \text{constant}$$
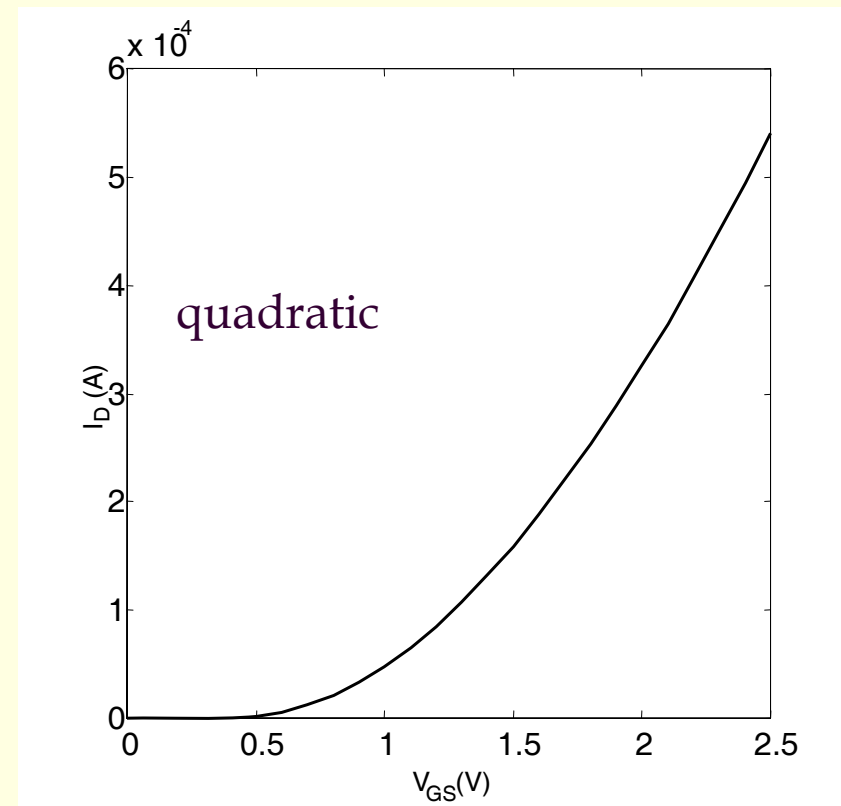
$$I_D = \frac{k_n W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



Introduction – 9

Experimental setup

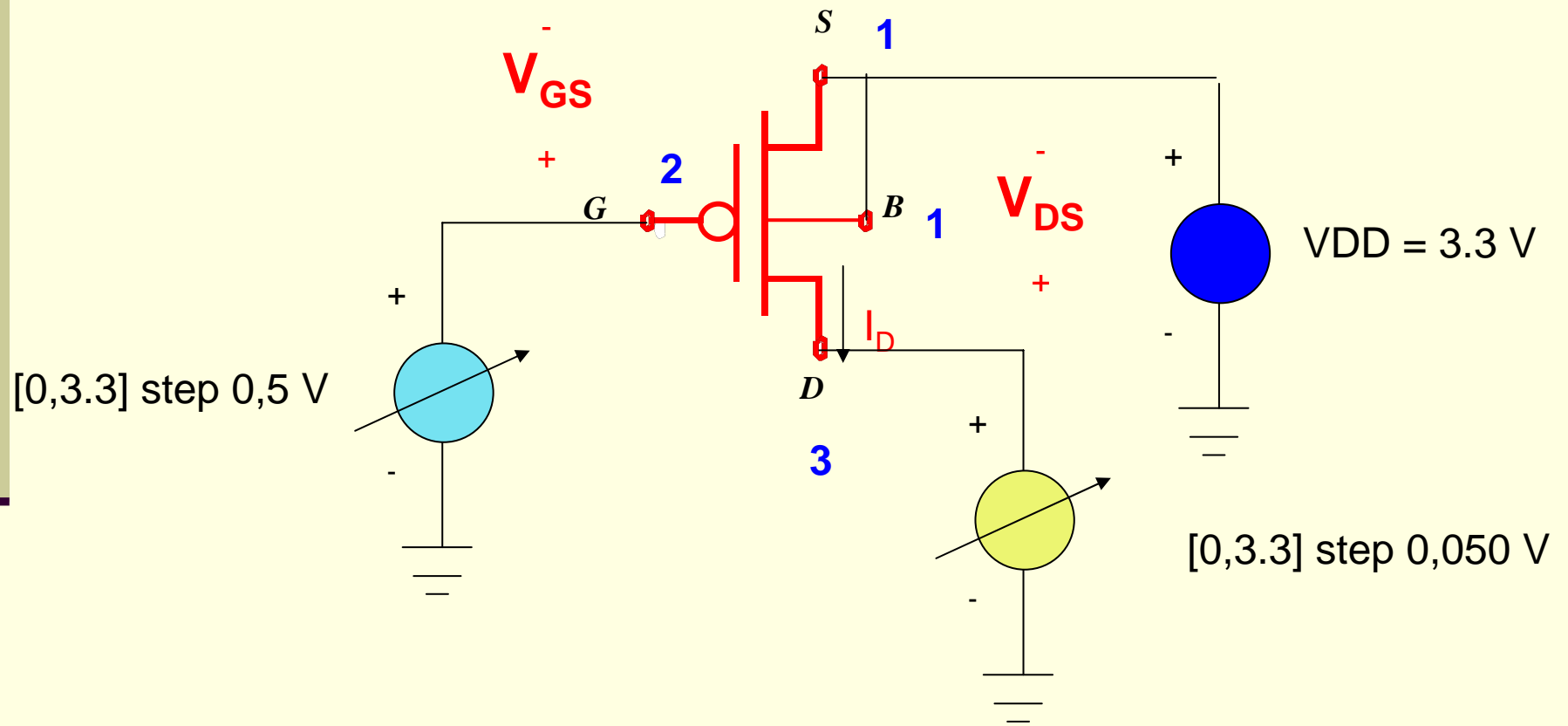


Introduction – 9

An experiment

- Circuit description (SPICE)
 - <http://www.inf.ufsc.br/~santos/ine5442/experiment/PMOSa.cir>
- Steps
 - <http://www.inf.ufsc.br/~santos/ine5442/experiment/roteiro.txt>


Introduction – 10

Simulation 6.1a
 $\lambda = 0.1$

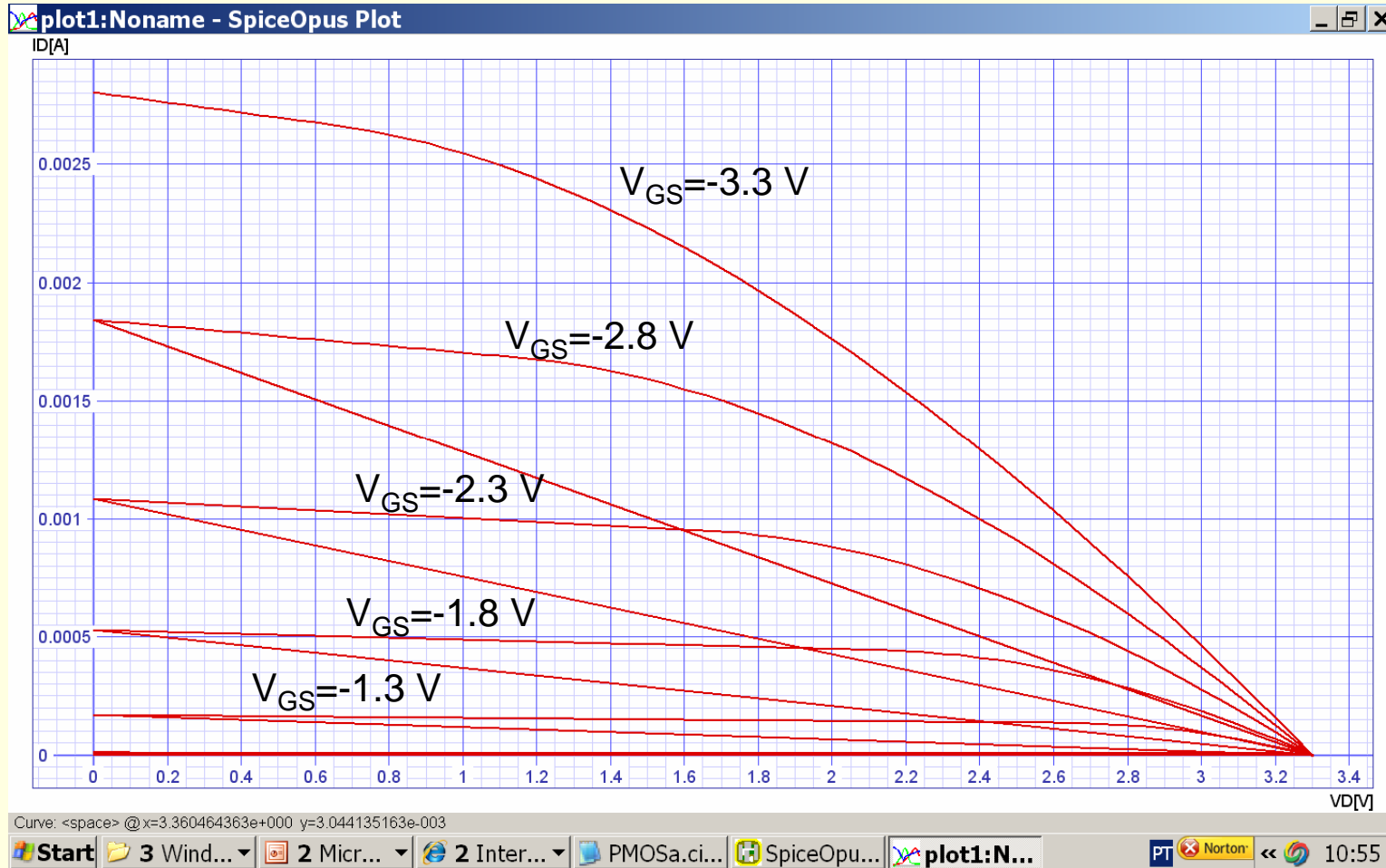

Introduction - 12


The Transistor as a Switch

 

$$R_{eq} \equiv \frac{1}{2}(R_0 + R_{mid})$$

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$
 
$$I_{DSAT} \equiv \frac{K_P}{2} \frac{W}{L} (V_{DD} - V_T)^2$$



Introduction - 13

CMOS static logic – the beginning

WEDNESDAY, FEBRUARY 20, 1963 ... UNIVERSITY OF PENNSYLVANIA—IRVINE AUDITORIUM ... 2:50-5:30 P.M.

SESSION III: Logic I

WPM 3.5: Nanowatt Logic Using Field-Effect Metal-Oxide Semiconductor Triodes

F. M. Wanlass and C. T. Sah

Fairchild Semiconductor Div., Fairchild Camera-Instrument Corporation

Palo Alto, Calif.

32 • 1963 *International Solid-State Circuits Conference*

Introduction - 14

CMOS static logic – the beginning

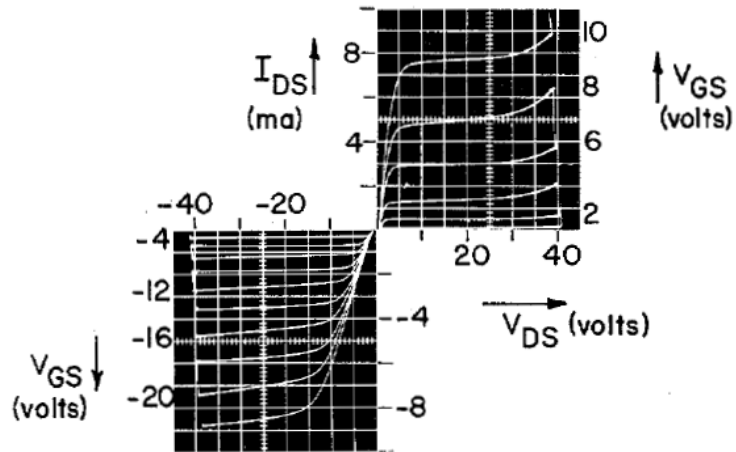


FIGURE 3—Characteristic curves for the field-effect triodes where drain current is plotted against drain voltage for source grounded and for different values of gate bias. The N element curves are plotted in the first quadrant.

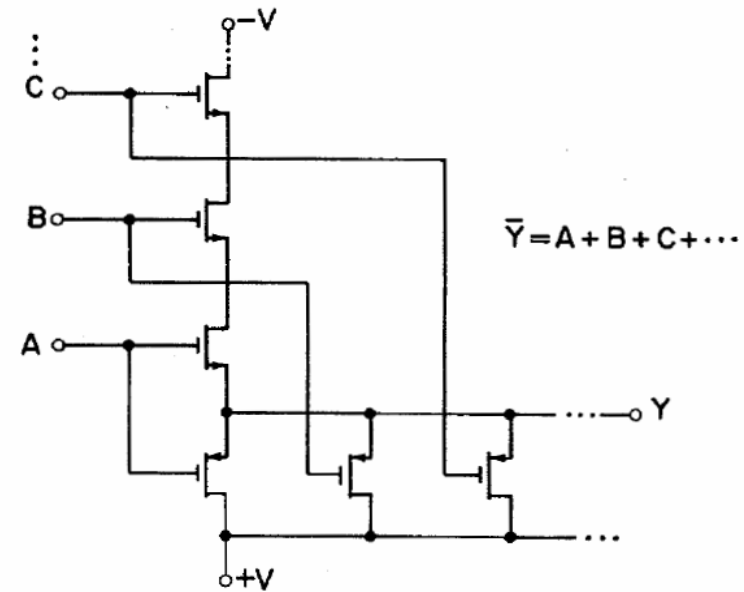


FIGURE 7—NOR logic circuit. If any of the inputs are $+V$ then the output will be $-V$.


 


FIGURE 4—Low standby power inverter circuit; when $V_i = +V$, $V_o = -V$ and when $V_i = -V$, $V_o = +V$.

Introduction - 15


 


CMOS device structure from Frank Wanlass's patent drawing.
U. S. Patent Office.




Introduction - 16

Schematic and layout - 1

  


Source: Rabaey

Introduction - 17 Schematic and layout -2

 


Figs 1.34–1.35(a) Inverter Cross-Section and Top View

Static characteristics - 1

 

V_{in}	0	V_{DD}
NMOS	OFF	ON
PMOS	ON	OFF
V_{out}	V_{DD}	0

 


$$V_{in} = V_{DD}$$


$$V_{GSn} = V_{DD} > V_{Tn}$$

$$V_{GSp} = 0 > V_{Tp}$$

Static characteristics - 1

 

V_{in}	0	V_{DD}
NMOS	OFF	ON
PMOS	ON	OFF
V_{out}	V_{DD}	0

 


$$V_{in} = 0$$


$$V_{GSn} = 0 < V_{Tn}$$

$$V_{GSp} = -V_{DD} < V_{Tp}$$

Static characteristics - 1

 


V_{in}	0	V_{DD}
NMOS	OFF	ON
PMOS	ON	OFF
V_{out}	V_{DD}	0

 

$$V_{in} = V_{DD}$$

$$V_{GSn} = V_{DD} > V_{Tn}$$

$$V_{GSp} = 0 > V_{Tp}$$

 


$$V_{in} = 0$$

$$V_{GSn} = 0 < V_{Tn}$$

$$V_{GSp} = -V_{DD} < V_{Tp}$$

Static characteristics - 2

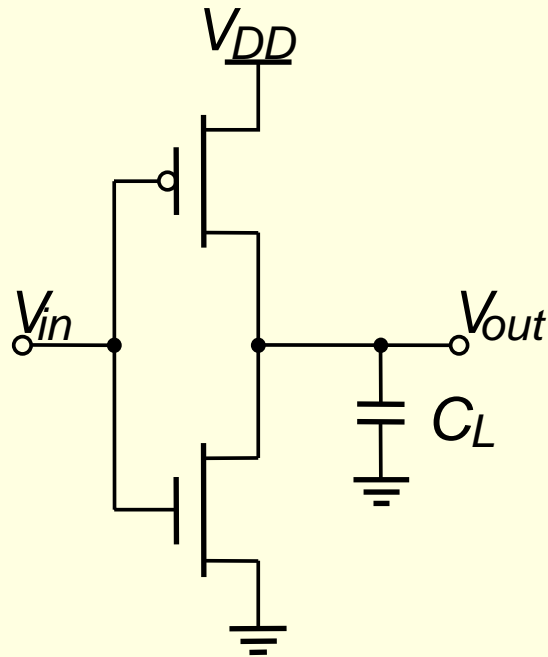

Voltage swing is equal to the supply voltage;


Logic levels are not dependent upon the relative device sizes;

In steady state there always exists a path with finite resistance between the output and either V_{DD} or ground;

The input resistance $\rightarrow \infty$;



No direct path exists between supply and ground rails under steady-state operating conditions (this is first order approx. and is far from reality in more advanced technologies) \rightarrow static power ≈ 0

Static characteristics - 3

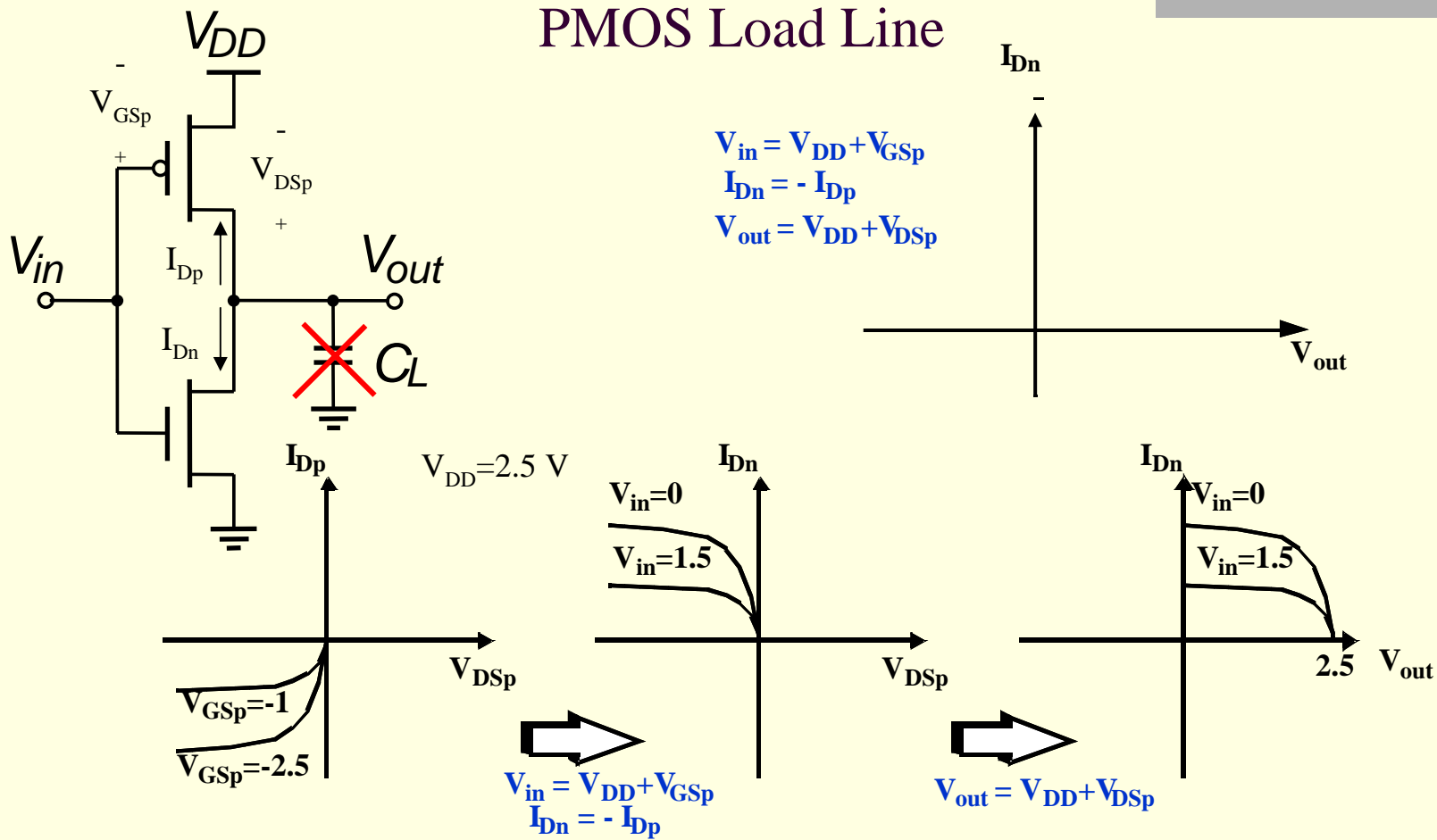

Static characteristics - 4

VTC

  

Source: Rabaey