



Digital Integrated Circuits A Design Perspective

Semiconductor Memories


Reference: Digital Integrated Circuits,
2nd edition, Jan M. Rabaey, Anantha
Chandrakasan and Borivoje Nikolic

Disclaimer: slides adapted for
INE5442/EEL7312 by José L. Güntzel
from the book's companion slides made
available by the authors.

Lecture Summary

- Memory Classification**
- Memory Architectures**
- The Memory Core (ROM Memories)**


Memory Timing: Definitions

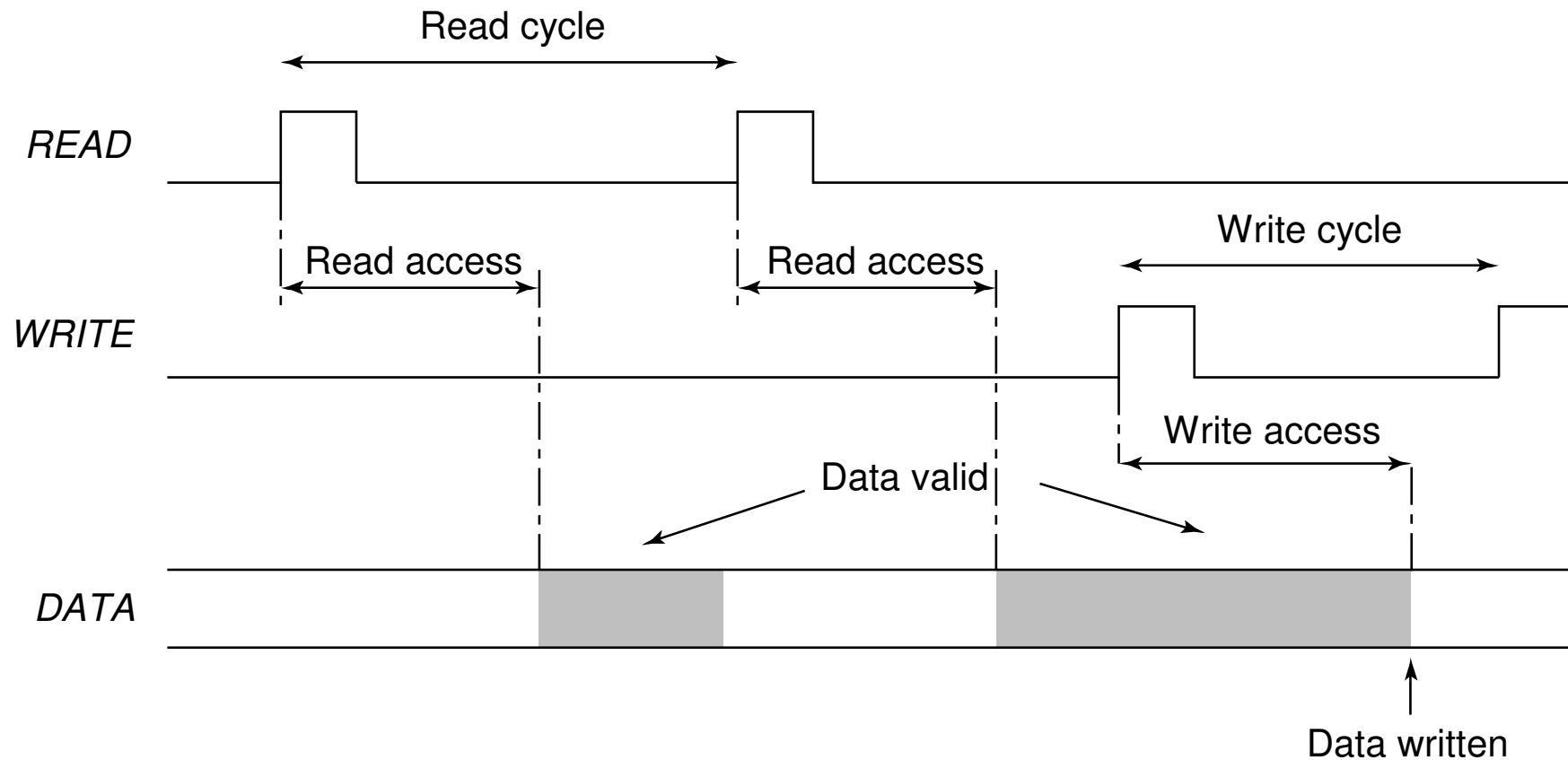


Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E ² PROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CAM		

Memory Architecture: Decoders

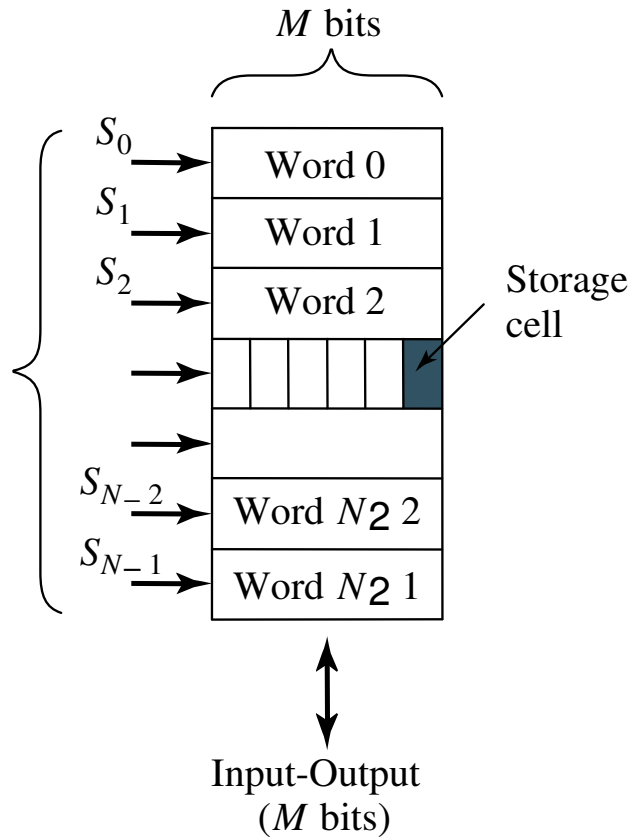

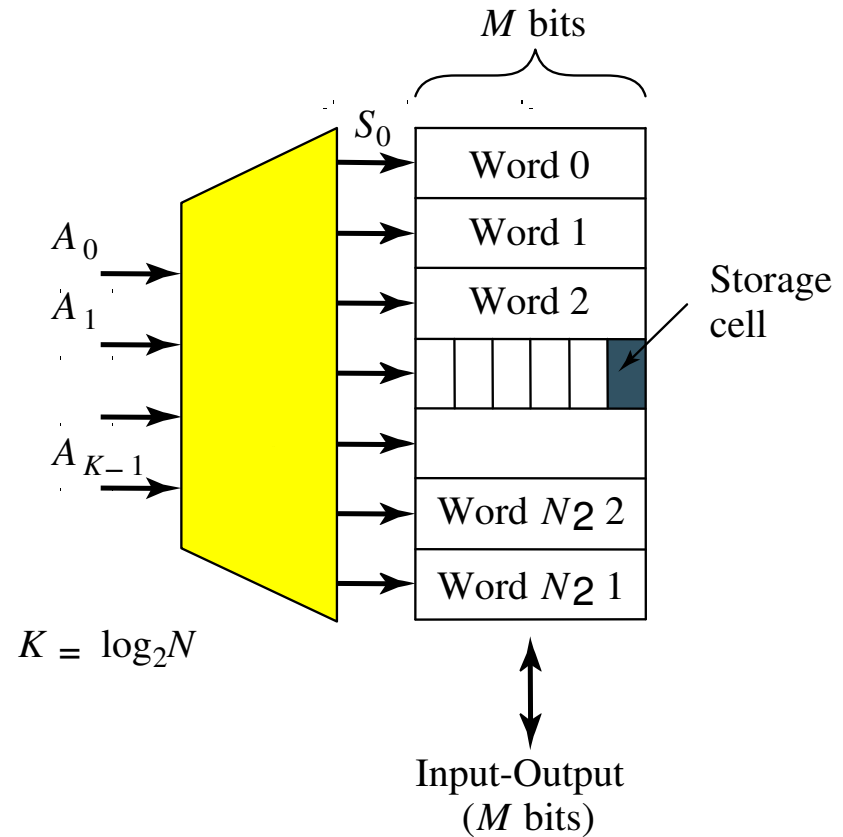
Intuitive architecture for $N \times M$ memory
 Too many select signals:
 N words == N select signals




Decoder reduces the number of select signals
 $K = \log_2 N$

Array-Structured Memory Architecture

 Problem: ASPECT RATIO or HEIGHT \gg WIDTH




Hierarchical Memory Architecture

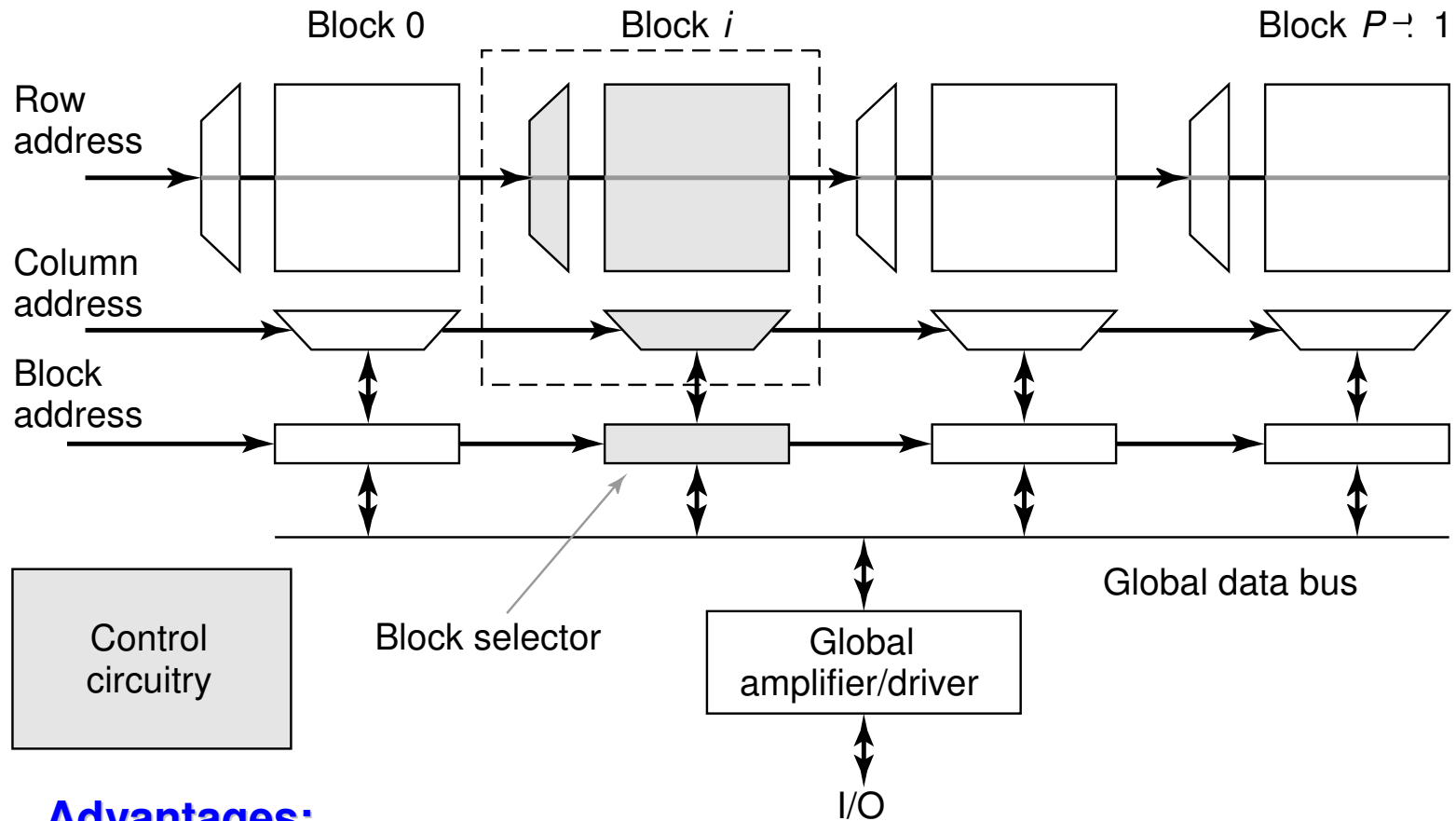


Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

Block Diagram of 4 Mbit SRAM

 


Contents-Addressable Memory

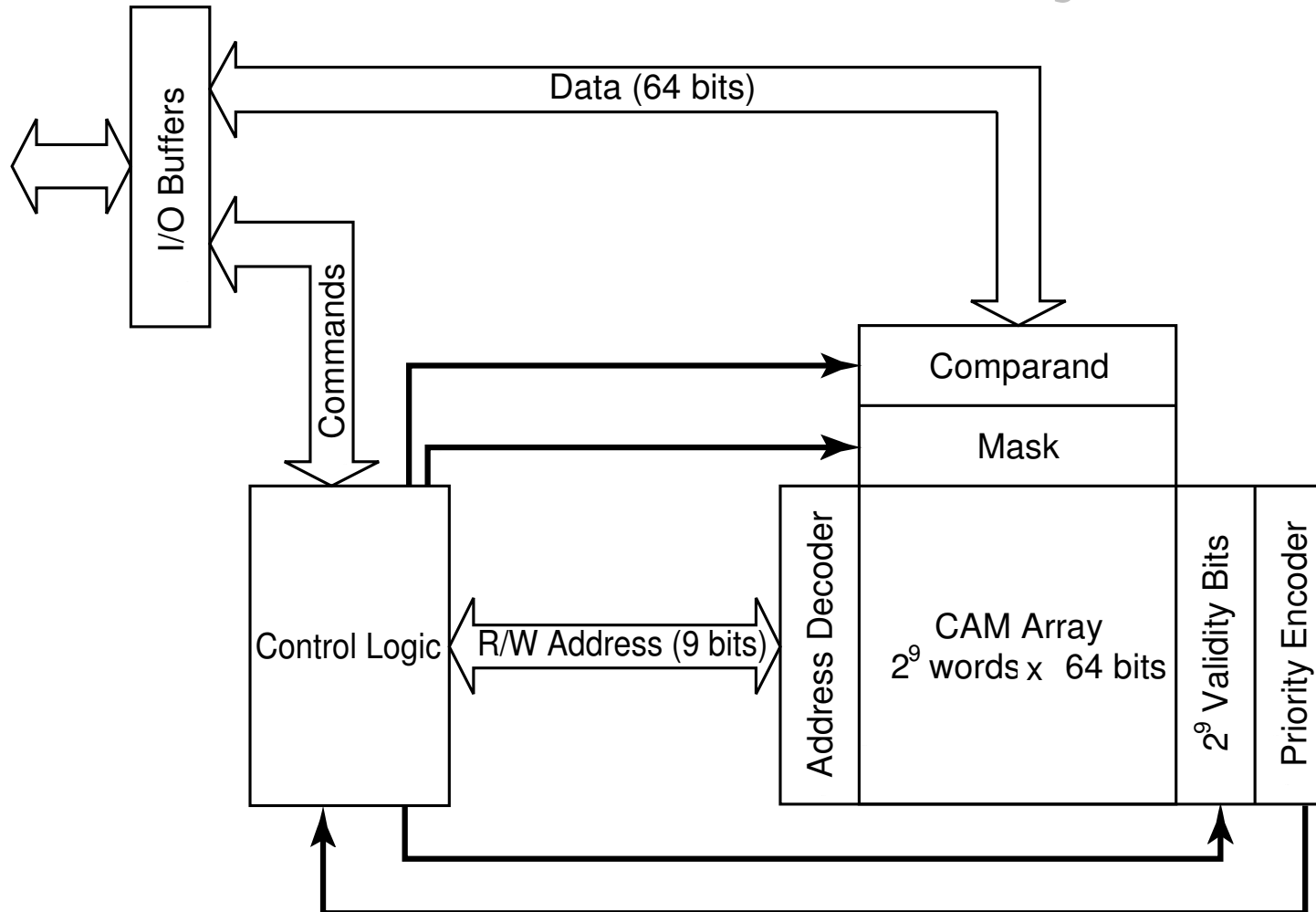

Memory Timing: Approaches

DRAM Timing Multiplexed Addressing

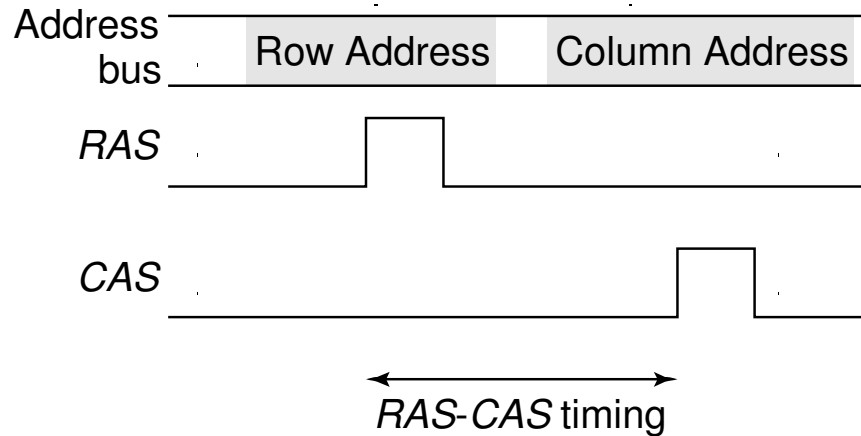


DRAM external timing signals:

RAS= Row Address Strobe


CAS=Column Address Strobe

SRAM Timing Self-timed

 


SRAM: no external timing signals!





Read-Only Memory Cells

 

Diode ROM

 


MOS ROM 1

    


MOS ROM 2

MOS ROM1: BL must be resistively clamped to ground
MOS ROM2: BL must be resistively clamped to Vdd

MOS OR ROM

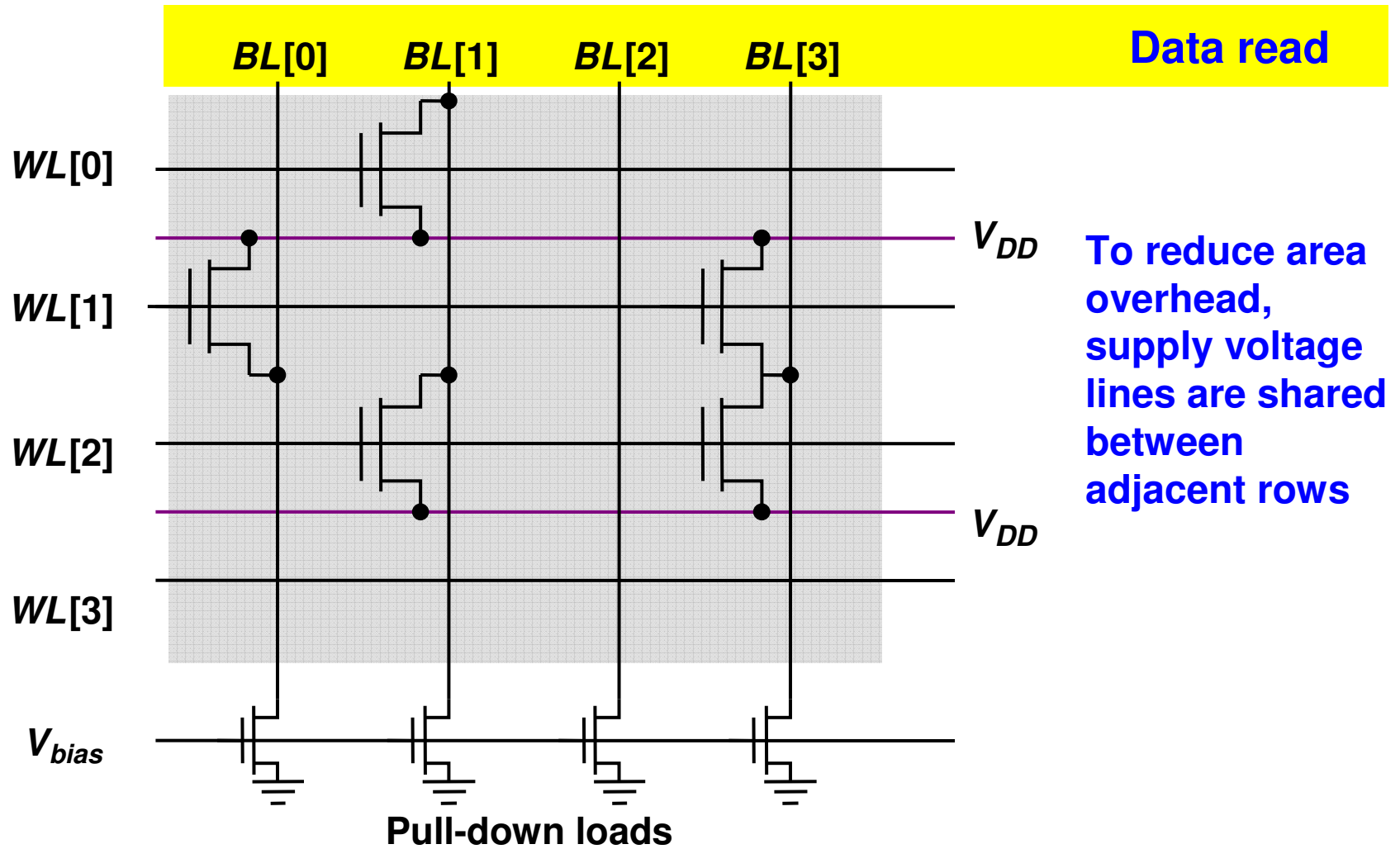


MOS NOR ROM

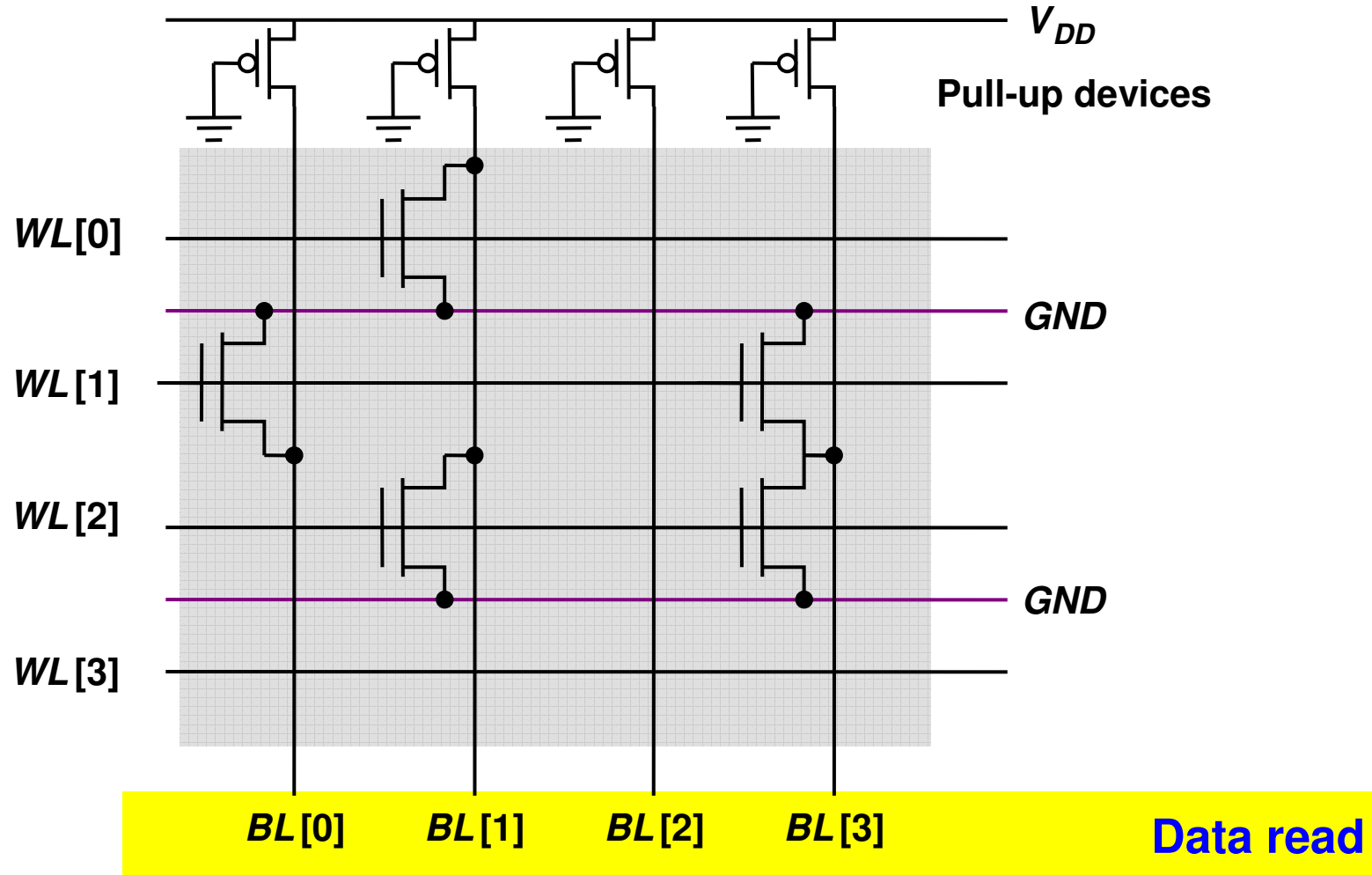


Each row is a pseudo-NMOS (WLs are the inputs)!

MOS NOR ROM Layout

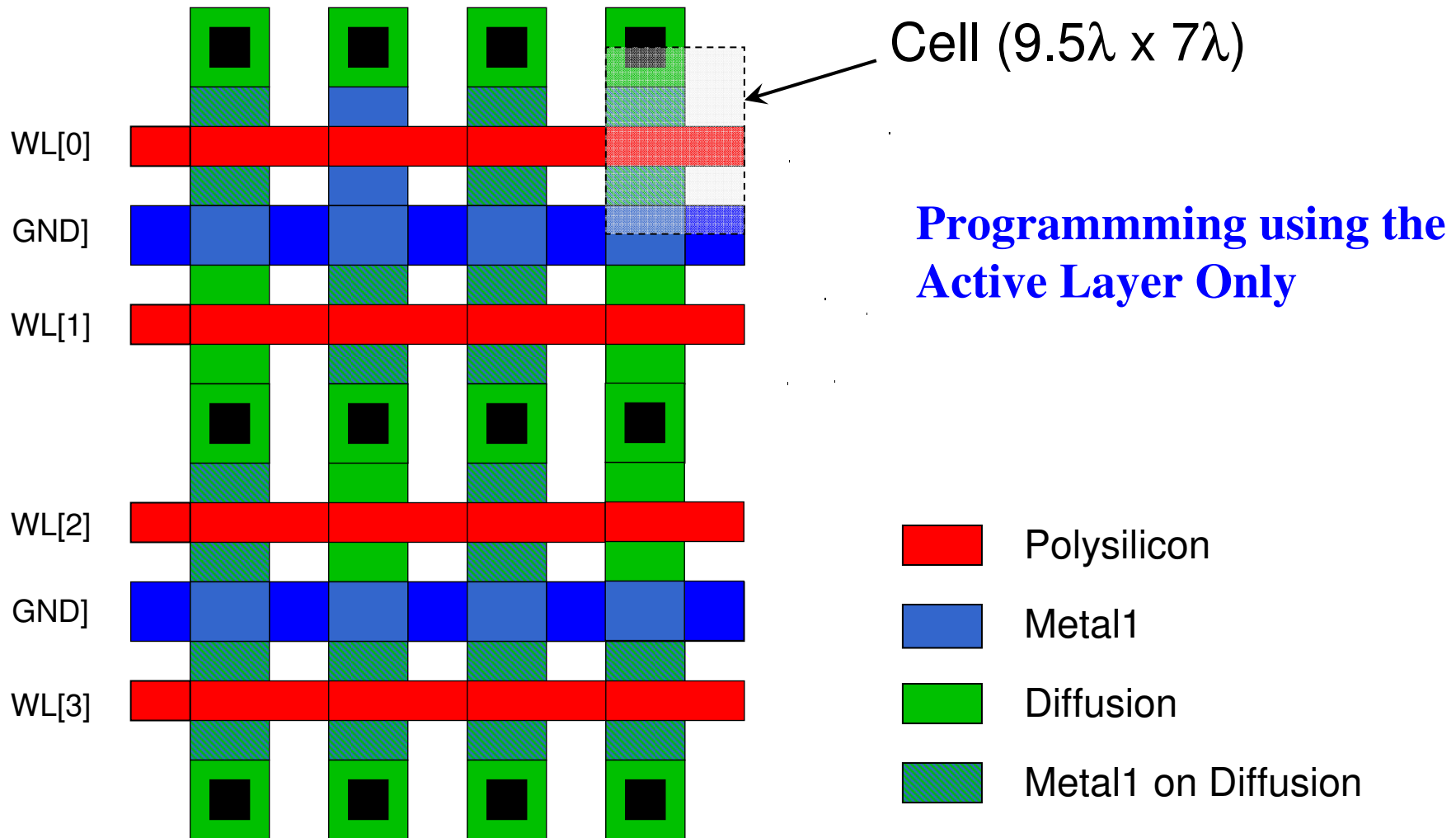

MOS NOR ROM Layout


Cell ($11\lambda \times 7\lambda$)

 

**Programmming using
the Contact Layer Only**


- Polysilicon
- Metal1
- Diffusion
- Metal1 on Diffusion

MOS NAND ROM

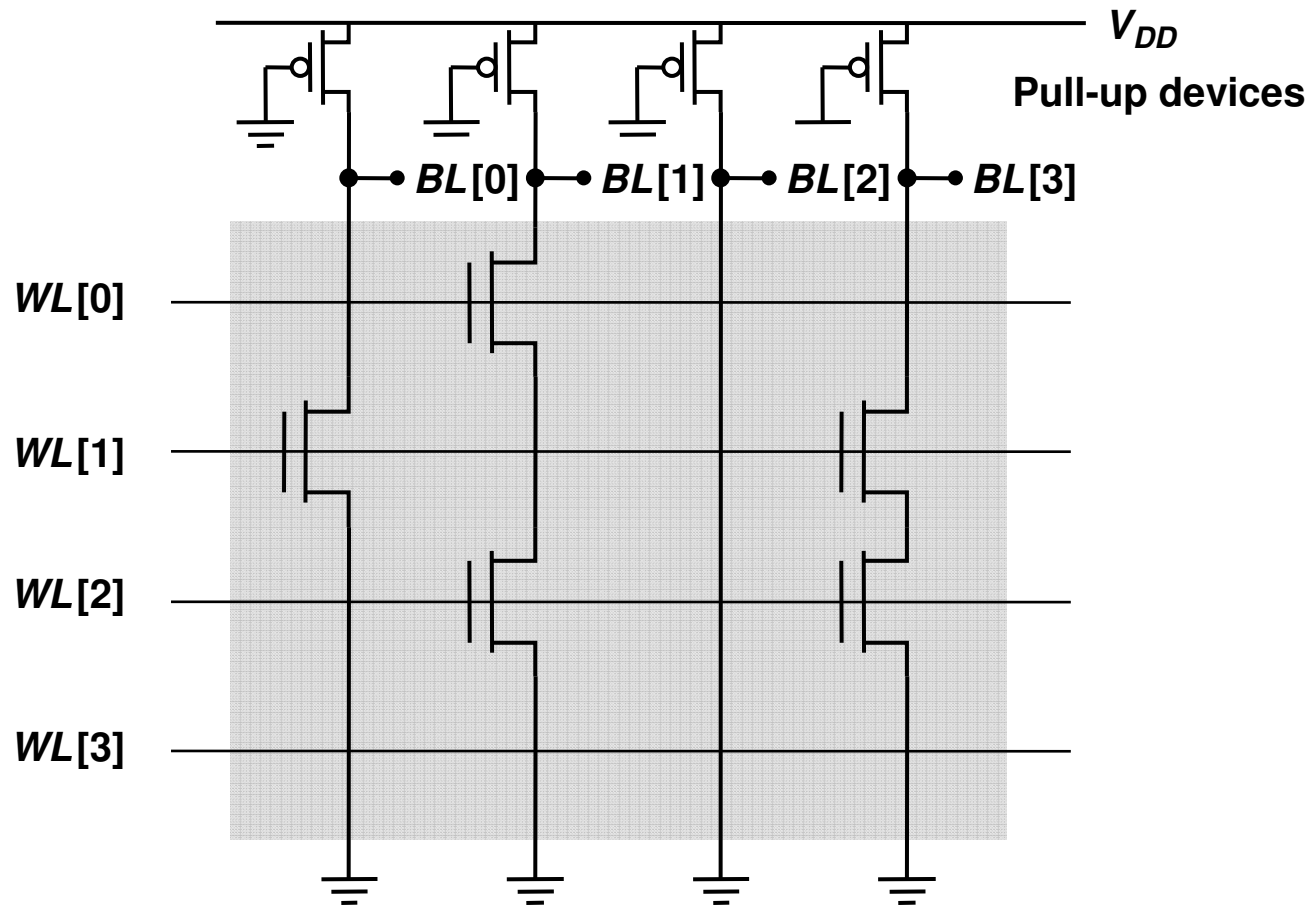

 All word lines high by default with exception of selected row




MOS NAND ROM Layout



Cell ($8\lambda \times 7\lambda$)


**Programmming using
the Metal-1 Layer Only**

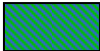**No contact to VDD or GND necessary;
drastically reduced cell size
Loss in performance compared to NOR ROM**




-  Polysilicon
-  Diffusion
-  Metal1 on Diffusion

NAND ROM Layout

 Cell ($5\lambda \times 6\lambda$)




**Programmming using
Implants Only**

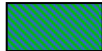-  Polysilicon
-  Threshold-altering implant
-  Metal1 on Diffusion

Equivalent Transient Model for MOS NOR ROM


Model for NOR ROM

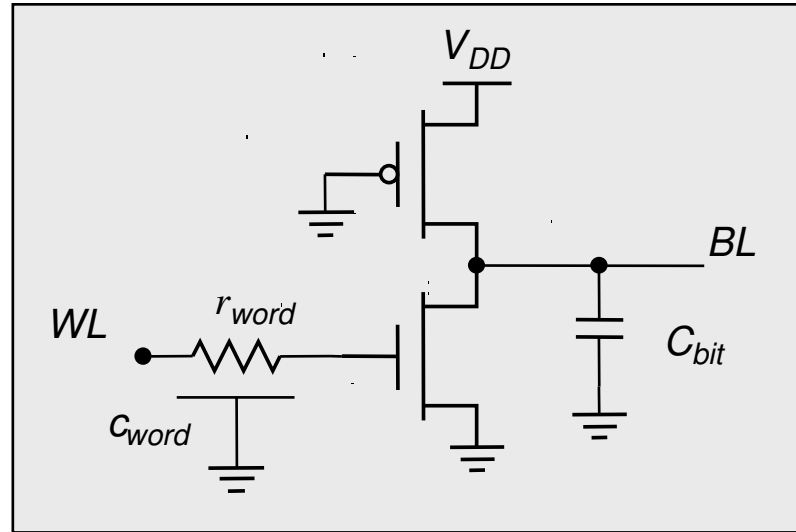

- Word line parasitics
 - Wire capacitance and gate capacitance
 - Wire resistance (polysilicon)
- Bit line parasitics
 - Resistance not dominant (metal)
 - Drain and Gate-Drain capacitance


Equivalent Transient Model for MOS NAND ROM

Model for NAND ROM

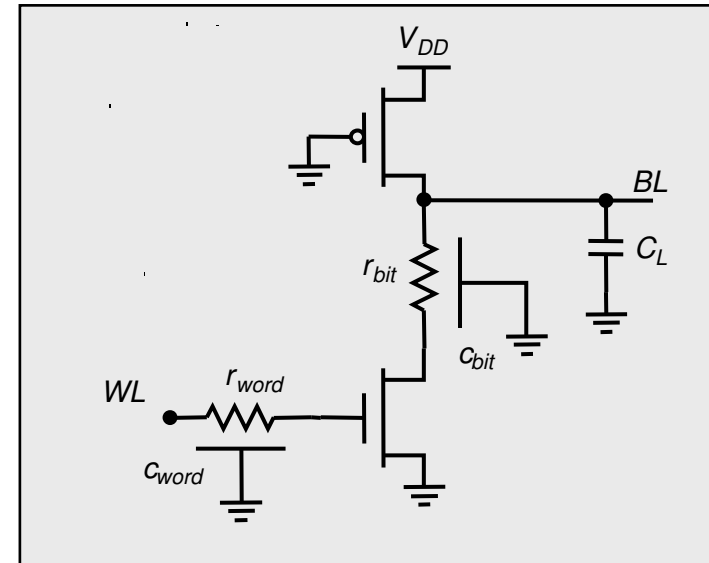


- ❑ Word line parasitics
 - Similar to NOR ROM
- ❑ Bit line parasitics
 - Resistance of cascaded transistors dominates
 - Drain/Source and complete gate capacitance

Decreasing Word Line Delay

 

 
(a) Driving the word line from both sides



(b) Using a metal bypass

(c) Use silicides

Precharged MOS NOR ROM

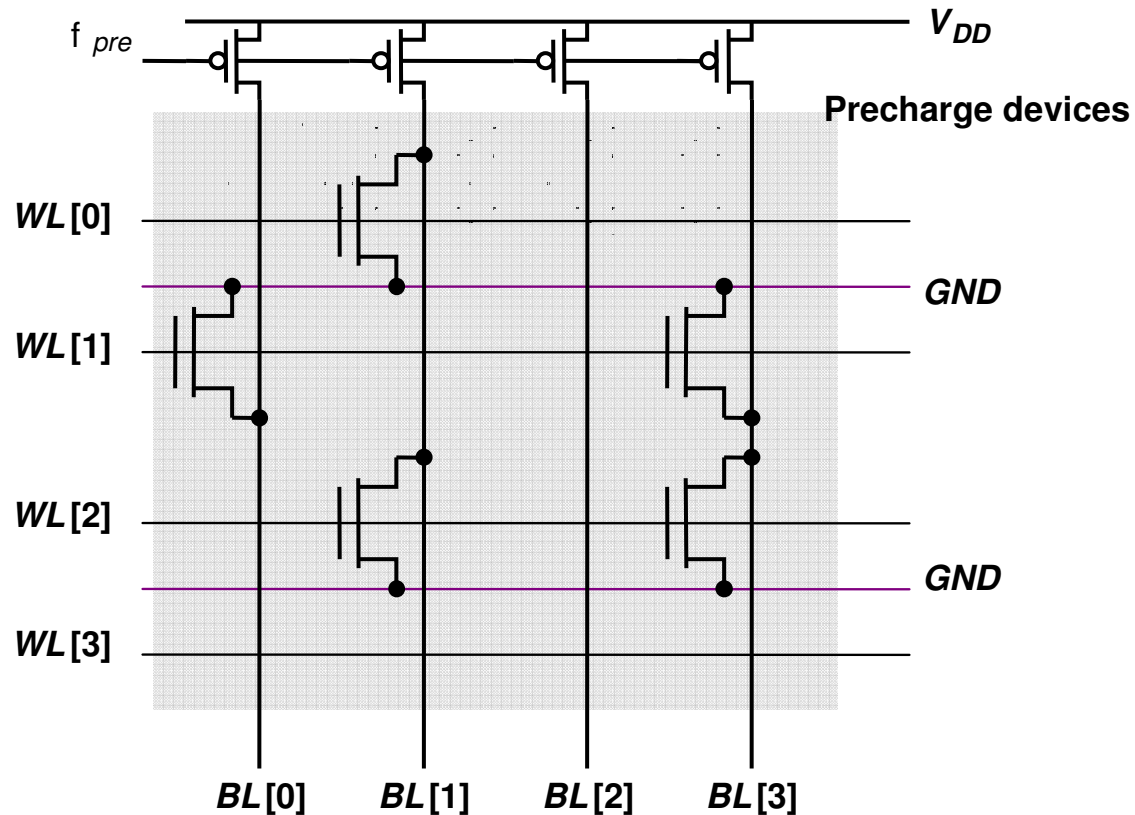

PMOS precharge device can be made as large as necessary, but clock driver becomes harder to design.